

Important note: *denotes questions that may require knowledge from later chapters in order to solve them.

I. MCQs (ACJC – MI)

1. [CJC/H2/Prelims 2018/P1/19]

The electrical potential difference between two points in a wire carrying a current is

- A the ratio of the power supplied to the current between the points.
- B the force required to move a unit positive charge between the points.
- C the ratio of the energy dissipated to the current between the points.
- D the product of the square of the current and the resistance between two points.

2. [CJC/H2/Prelims 2018/P1/20]

An electrical source with internal resistance r is used to operate a lamp of resistance R .

What fraction of the total power is delivered to the lamp?

- A $\frac{R+r}{R}$
- B $\frac{R-r}{R}$
- C $\frac{R}{R+r}$
- D $\frac{R}{r}$

3. [CJC/H2/Prelims 2018/P1/21]


A high potential is applied between the electrodes of a hydrogen discharge tube so that the gas is ionised. Electrons then move towards the positive electrode and protons towards the negative electrode. In each second, 7×10^{18} electrons and 2×10^{18} protons pass a cross section of the tube.

The current flowing in the discharge tube is

- A 0.32 A
- B 0.80 A
- C 1.12 A
- D 1.44 A

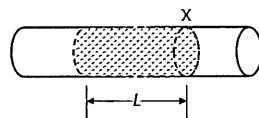4. [EJC/H2/Prelims 2018/P1/19]

A copper wire has a number density of 8.5×10^{28} conduction electrons per cubic metre, and an cross-sectional area of $3.2 \times 10^{-7} \text{ m}^2$. When a potential difference is applied to the ends of the wire, the current is 1.0 A.



If all the electrons within a cylinder of length L pass point X in 60 s, what is the value of L ?

- A 0.00015 m
- B 0.014 m
- C 0.025 m
- D 0.20 m

5. [JJC/H2/Prelims 2018/P1/18]

The current in a component is reduced uniformly from 100 mA to 20 mA over a period of 8.0 s.

What is the charge that flows during this time?

- A 160 mC
- B 320 mC
- C 480 mC
- D 640 mC

6. [RVHS/H2/Prelims 2018/P1/18]


A uniform copper rod of cross-sectional area $8.0 \times 10^{-6} \text{ m}^2$ has 8.5×10^{28} conduction electrons per cubic metre. Current flows through the rod when a potential difference is applied across it.

Given that the drift velocity of electrons in the rod is $2.3 \times 10^{-5} \text{ m s}^{-1}$, what is the current in the rod?

- A 0.25 A
- B 0.40 A
- C 2.5 A
- D 4.0 A

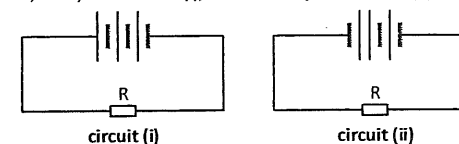7. [VJC/H2/Prelims 2018/P1/20]

Three identical cells each having an e.m.f. of 1.5 V and a constant internal resistance of 2.0Ω are connected in series with a 4.0Ω resistor R, firstly as in circuit (i), and secondly as in circuit (ii).



What is the ratio $\frac{\text{power in R in circuit (i)}}{\text{power in R in circuit (ii)}}$?

- A 9.0
- B 7.2
- C 5.4
- D 3.0

8. [YJC/H2/Prelims 2018/P1/24]


A wire has diameter 0.35 mm and the number density of charge carriers is $7.8 \times 10^{28} \text{ m}^{-3}$. The current in the wire is 0.15 A.

What is the drift velocity of the charge carriers?

- A $1.2 \times 10^{-18} \text{ m s}^{-1}$
- B $3.1 \times 10^{-11} \text{ m s}^{-1}$
- C $3.1 \times 10^{-5} \text{ m s}^{-1}$
- D $1.2 \times 10^{-4} \text{ m s}^{-1}$

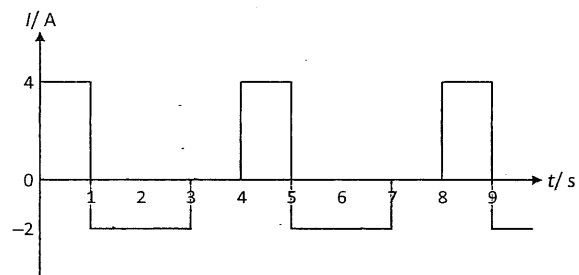9. [AJC/H2/Prelims 2018/P1/25]

An alternating current with a rectangular waveform as shown below flows through an $11\ \Omega$ resistor.




What is the average power dissipated by the resistor?

- A 0 W B 44 W C 66 W D 88 W

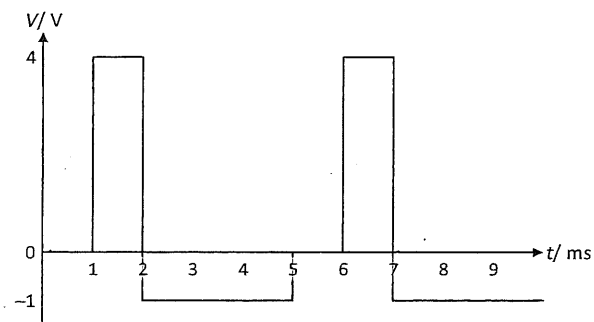10. [AJC/H2/Prelims 2018/P1/24]

The variation with time t of the voltage V of an alternating source applied across a $2.0\ \Omega$ resistor is shown below.




What is the power dissipated in the resistor?

- A 0.98 W B 1.5 W C 1.9 W D 2.4 W

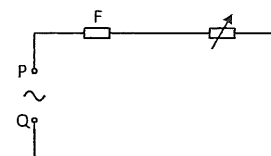11. [CJC/H2/Prelims 2018/P1/23]

When an alternating power supply of 240 V r.m.s. is connected across PQ in the circuit shown below.



The fuse F breaks the circuit if the current in it just exceeds 13 A r.m.s.

When the alternating power supply is replaced with a 120 V d.c. source, an identical fuse breaks the circuit if the current just exceeds

- A $\frac{13}{2}$ A B $\frac{13}{\sqrt{2}}$ A C 13 A D 26 A

12. [CJC/H2/Prelims 2018/P1/24]

An alternating power supply of root-mean-square voltage 4.0 V is connected across a resistive load such that the average power dissipated across it is P .

What is the d.c. voltage applied across the same load which will give rise to an average power dissipation of $3P$?

- A 6.9 V B 8.5 V C 12 V D 17 V

13. [DHS/H2/Prelims 2018/P1/26]


A sinusoidal alternating current of peak value I_0 passes through a resistor of resistance R . The mean power developed by the current in the resistor is P .

Another sinusoidal alternating current passes through a resistor of resistance $2R$. If the mean power developed by this current in it is $4P$, what is the root-mean-square value of this current?

- A $0.7I_0$ B I_0 C $1.4I_0$ D $2.0I_0$

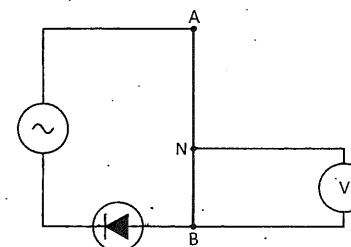14. [EJC/H2/Prelims 2018/P1/24 Modified]

The uniform wire AB has length 1.0 m and resistance of $10\ \Omega$. When NB is 40.0 cm, the a.c. voltmeter reads a steady r.m.s. voltage of 2.5 V.



What is the peak power provided by the supply?

- A 0.63 W B 3.9 W C 7.8 W D 16 W

3. [YJC/H2/Prelims 2018/P3/7]

- a. Domestic users in the United Kingdom are supplied with mains electricity at a root-mean-square voltage (r.m.s.) of 230 V.
- State what is meant by root-mean-square voltage. [1]
 - Calculate the peak power dissipated in a lamp connected to the mains supply when the r.m.s. current is 0.26 A. [2]
- b. Another alternating voltage is shown in Fig. 7.1.

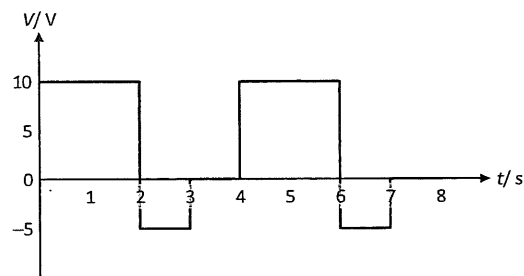


Fig. 7.1

Determine the root-mean-square voltage.

[2]

[Total: 5]

